

VERILOG

Hardware Description Language

Courtesy: Prof. Indranil Sengupta

About Verilog

- Along with VHDL, Verilog is among the most widely used HDLs.
- Main differences:
 - VHDL was designed to support system-level design and specification.
 - Verilog was designed primarily for digital hardware designers developing FPGAs and ASICs.
- The differences become clear if someone analyzes the language features.

- **VHDL**

- Provides some high-level constructs not available in Verilog (user defined types, configurations, etc.).

- **Verilog**

- Provides comprehensive support for low-level digital design.
 - Not available in native VHDL
 - Range of type definitions and supporting functions (called packages) needs to be included.

Concept of Verilog “Module”

- In Verilog, the basic unit of hardware is called a module.
 - Modules cannot contain definitions of other modules.
 - A module can, however, be instantiated within another module.
 - Allows the creation of a *hierarchy* in a Verilog description.

Basic Syntax of Module Definition

```
module module_name (list_of_ports);
```

```
    input/output declarations
```

```
    local net declarations
```

```
    Parallel statements
```

```
endmodule
```

Example 1 :: simple AND gate

```
module simpleand (f, x, y);  
    input x, y;  
    output f;  
    assign f = x & y;  
endmodule
```

Example 2 :: two-level circuit

```
// Dataflow modeling example
module two_level (a, b, c, d, f);
    input  a, b, c, d;
    output f;
    wire t1, t2;
    assign t1 = a & b;
    assign t2 = ~ (c | d);
    assign f = t1 ^ t2;
endmodule
```

Example 3 :: a hierarchical design

// Structural modeling example

```
module add3 (s, cy3, cy_in, x, y);  
    input [2:0] x, y;  
    input cy_in;  
    output wire [2:0] s;  
    output wire cy3;  
    wire [1:0] cy_out;  
    add B0 (cy_out[0], s[0], x[0], y[0], cy_in);  
    add B1 (cy_out[1], s[1], x[1], y[1], cy_out[0]);  
    add B2 (cy3, s[2], x[2], y[2], cy_out[1]);  
endmodule
```

// Somewhere “add” module (full adder) has been defined...

```
module add (cout, sum, in1, in2, cin);  
    input in1, in2, cin;  
    output wire sum, cout;  
    .....  
endmodule
```


Specifying Connectivity

- There are two alternate ways of specifying connectivity:
 - Positional association
 - The connections are listed in the same order
add A1 (c_out, sum, a, b, c_in);
 - Explicit association [Highly recommended!!]
 - May be listed in any order
add A1 (.in1(a), .in2(b), .cin(c_in),
.sum(sum), .cout(c_out));

Variable Data Types

- A variable belongs to one of two data types:
 - Net
 - Must be continuously driven
 - Used to model connections between continuous assignments & instantiations
 - Register
 - Retains the last value assigned to it
 - Often used to represent storage elements
 - However, combinational circuits can also be represented using the “reg” keyword
 - In practice: a “reg” type variable is one that occurs on the left-hand side of value assignment statements inside an “always” block

Net data type

- Different ‘net’ types supported for synthesis:
 - *wire, wor, wand, tri, supply0, supply1*
- ‘wire’ and ‘tri’ are equivalent; when there are multiple drivers driving them, the outputs of the drivers are shorted together.
- ‘wor’ / ‘wand’ inserts an OR / AND gate at the connection.
- ‘supply0’ / ‘supply1’ model power supply connections.

```
module using_wire (A, B, C, D, f);  
    input  A, B, C, D;  
  
    output wire f; // net f declared as 'wire'  
  
    assign f = (A & B) ^ (~(C | D));  
  
endmodule
```

```
module using_supply_wire (A, B, C, f);  
    input    A, B, C;  
    output   wire f;  
    supply0  gnd;  
    supply1  vdd;  
    wire t1, t2;  
  
    nand G1 (t1, vdd, A, B);  
    xor   G2 (t2, C, gnd);  
    and   G3 (f, t1, t2);  
endmodule
```

Register data type

- Different ‘register’ types supported for synthesis:
 - reg, integer
- The ‘reg’ declaration explicitly specifies the size.
 - reg x, y; // single-bit register variables
 - reg [15:0] bus; // 16-bit bus, bus[15] MSB
- For ‘integer’, it takes the default size, usually 32-bits.
 - Synthesizer tries to determine the size.

Other differences:

- **In arithmetic expressions,**
 - An 'integer' is treated as a 2's complement signed integer.
 - A 'reg' is treated as an unsigned quantity.
- **General rule of thumb**
 - 'reg' used to model actual hardware registers such as counters, accumulator, etc.
 - 'integer' used for situations like loop counting.

```
// Behavioral modeling, synchronous reset  
module simple_counter (clk, rst, count);  
    input  clk, rst;  
    output reg [31:0] count;  
// Sensitivity list contains only clk  
    always @(posedge clk)  
    begin  
        if (rst)  
            count = 32'b0;  
        else  
            count = count + 1;  
    end  
endmodule
```



```
// Behavioral modeling, asynchronous reset  
module simple_counter (clk, rst, count);  
    input  clk, rst;  
    output reg [31:0] count;  
// Sensitivity list contains both clk and rst  
always @(posedge clk or posedge rst)  
    begin  
        if (rst)  
            count = 32'b0;  
        else  
            count = count + 1;  
    end  
endmodule
```

- When 'integer' is used, the synthesis system often carries out a data flow analysis of the model to determine its actual size.

- Example:

```
wire [1:10] A, B;  
integer    C;  
C = A + B;
```

→ The size of C can be determined to be equal to 11 (10 bits plus a carry).

Specifying Constant Values

- A value may be specified in either the 'sized' or the 'un-sized' form.
- 'size' denotes the no. of bits
 - Syntax for 'sized' form:
`<size>'<base><number>`
- Examples:
 - `8'b01110011` // 8-bit binary number
 - `12'hA2D` // 1010 0010 1101 in binary
 - `12'hCx5` // 1100 xxxx 0101 in binary
 - `25` // signed number, 32 bits
 - `1'b0` // logic 0
 - `1'b1` // logic 1

Parameters

- A *parameter* is a constant with a name.
- No size is allowed to be specified for a parameter.
 - The size gets decided from the constant itself (32-bits if nothing is specified).
- Examples:
 - parameter HI = 25, LO = 5;
 - parameter up = 2b'00, down = 2b'01,
steady = 2b'10;

Logic Values

- The common values used in modeling hardware are:
 - 0 :: Logic-0 or FALSE
 - 1 :: Logic-1 or TRUE
 - x :: Unknown (or don't care)
 - z :: High impedance
- Initialization:
 - All unconnected nets set to 'z'
 - All register variables set to 'x'

- Verilog provides a set of predefined logic gates.
 - They respond to inputs (0, 1, x, or z) in a logical way.
 - Example :: AND

0 & 0 → 0

0 & 1 → 0

1 & 1 → 1

1 & x → x

0 & x → 0

1 & z → x

z & x → x

Primitive Gates

- **Primitive logic gates (instantiations):**

and **G (out, in1, in2);**

nand **G (out, in1, in2);**

or **G (out, in1, in2);**

nor **G (out, in1, in2);**

xor **G (out, in1, in2);**

xnor **G (out, in1, in2);**

not **G (out1, in);**

buf **G (out1, in);**

- **Primitive Tri-State gates (instantiation)**

bufif1 G (out, in, ctrl);

bufif0 G (out, in, ctrl);

notif1 G (out, in, ctrl);

notif0 G (out, in, ctrl);

Some Points to Note

- For all primitive gates,
 - The output port must be connected to a net (a wire).
 - The input ports may be connected to nets or register type variables.
 - They can have a single output but any number of inputs.
 - An optional delay may be specified.
 - *Logic synthesis tools ignore time delays.*

```
`timescale 1 ns / 1ps  
module exclusive_or (f, a, b);  
    input a, b;  
    output f;  
    wire t1, t2, t3;  
    nand #5 m1 (t1, a, b);  
    and #5 m2 (t2, a, t1);  
    and #5 m3 (t3, t1, b);  
    or #5 m4 (f, t2, t3);  
endmodule
```

Hardware Modeling Issues

- The values computed can be held in
 - A 'wire'
 - A 'flip-flop' (edge-triggered storage cell)
 - A 'latch' (level-sensitive storage cell)
- A variable in Verilog can be of
 - 'net data type'
 - Maps to a 'wire' during synthesis
 - 'register' data type
 - Maps either to a 'wire' or to a 'storage cell' depending on the context under which a value is assigned.

```
module reg_maps_to_wire (A, B, C, f1, f2);  
    input  A, B, C;  
    output reg f1, f2;  
  
    always @(A or B or C) // also possible: always @(*)  
    begin  
        // Blocking assignments  
        f1 = ~(A & B);  
        f2 = f1 ^ C;  
    end  
endmodule
```

The synthesis system
will generate a wire
for f1

```
module a_problematic_case (A, B, C, f1, f2);  
  input  A, B, C;  
  output f1, f2;  
  wire   A, B, C;  
  reg    f1, f2;  
  always @(A or B or C)  
  begin  
    f2 = f1 ^ f2;  
    f1 = ~(A & B);  
  end  
endmodule
```

The synthesis system
will not generate a
storage cell for f1

```
// A latch gets inferred here
module simple_latch (data, load, d_out);
    input  data, load;
    output reg d_out;
    reg t;
    always @(load or data)
    begin
        if (!load)
            t = data;
        d_out = !t;
    end
endmodule
```

Else part missing; so
latch is inferred.

Verilog Operators

- Arithmetic operators

$*, /, +, -, \%$

- Logical operators

$!$ \rightarrow logical negation

$\&\&$ \rightarrow logical AND

$||$ \rightarrow logical OR

- Relational operators

$>, <, >=, <=, ==, !=$

- Bitwise operators

$\sim, \&, |, ^, \sim^{\wedge}$

- Reduction operators (operate on all the bits within a word)

&, ~&, |, ~|, ^, ~^

➔ accepts a single word operand and produces a single bit as output

- Shift operators

>>, <<

- Concatenation { }
- Replication { { } }
- Conditional

<condition> ? <expression1> : <expression2>


```
module operator_example (x, y, f1, f2);  
    input    x, y;  
    output f1, f2, f3, f4;  
    wire [9:0] x, y;    wire [4:0] f1, f4;  
    wire f2, f3;  
  
    assign f1 = x[4:0] & y[4:0];  
    assign f2 = x[2] | ~f1[3];  
    assign f3 = ~& x;  
    assign f4 = f2 ? x[9:5] : x[4:0];  
endmodule
```

// An 8-bit adder description

```
module parallel_adder (sum, cout, in1, in2, cin);  
  input [7:0] in1, in2;  
  input cin;  
  output wire [7:0] sum;  
  output wire cout;  
  
  assign {cout, sum} = in1 + in2 + cin;  
endmodule
```

Some Points

- The presence of a 'z' or 'x' in a *reg* or *wire* being used in an arithmetic expression results in the whole expression being unknown ('x').
- The logical operators (!, &&, | |) all evaluate to a 1-bit result (0, 1 or x).
- The relational operators (>, <, <=, >=, ~=, ==) also evaluate to a 1-bit result (0 or 1).
- Boolean *false* is equivalent to 1'b0
Boolean *true* is equivalent to 1'b1.

Some Valid Statements

assign non_zero = |x; //non_zero is 1 if x is non-zero

assign outp = (p == 4'b1111);

if (load && (select == 2'b01))

assign a = b >> 1;

assign a = b << 3;

assign f = {a, b};

assign f = {a, 3'b101, b};

assign f = {x[2], y[0], a};

assign f = { 4{a} }; // same as {a, a, a, a}

assign f = {2'b10, 3{2'b01}, x};

Description Styles in Verilog

- **Two different styles of description:**
 1. **Data flow**
 - Continuous assignment
 2. **Behavioral**
 - Procedural assignment
 - ❖ Blocking
 - ❖ Non-blocking

Data-flow Style: Continuous Assignment

- Identified by the keyword “assign”.
 assign a = b & c;
 assign f[2] = c[0];
- Forms a static binding between
 - The ‘net’ being assigned on the LHS,
 - The expression on the RHS.
- The assignment is continuously active.
- Almost exclusively used to model combinational logic.

- A Verilog module can contain any number of continuous assignment statements, all of which are evaluated immediately whenever the value of the RHS expression changes.
- For an “assign” statement,
 - The expression on RHS may contain both “register” or “net” type variables.
 - The LHS must be of “net” type, typically a “wire”.
- Several examples of “assign” illustrated already.

```
module generate_mux (data, select, out);  
  input [7:0] data;  
  input [2:0] select;  
  output wire out;  
  
  assign out = data[select];  
endmodule
```

**Non-constant index in
expression on RHS
generates a MUX**


```
module generate_demultiplexer (out, in, select);  
  input in;  
  input [1:0] select;  
  output [3:0] out;  
  
  assign out[select] = in;  
endmodule
```

**Non-constant index in
expression on LHS
generates a demux**

```
module generate_MUX_2 (a, b, f, sel);  
    input [0:3] a, b;  
    input sel;  
    output [0:3] f;  
  
    assign f = sel ? a : b;  
endmodule
```


**Conditional operator
generates a 2:1 MUX**

Behavioral Style: Procedural Assignment

- The procedural block defines
 - A region of code containing *sequential* statements.
 - The statements execute in the order they are written.
- Two types of procedural blocks in Verilog
 - The “always” block
 - A continuous loop that never terminates.
 - The “initial” block
 - Executed once at the beginning of simulation (used in Test-benches).

- A module can contain any number of “always” blocks, all of which execute concurrently.
- Basic syntax of “always” block:
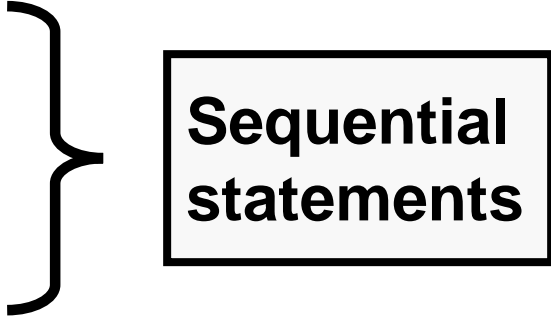
```
always @ (event_expression)
begin
    statement;
    statement;
end
```



The diagram shows a right-facing curly brace grouping the two 'statement;' lines in the code block above. To the right of the brace is a rectangular box with a black border containing the text 'Sequential statements'.

- The @(event_expression) is required for both combinational and sequential logic descriptions.

- Only “reg” type variables can be assigned within an “always” block.
Why??
 - The sequential “always” block executes only when the event expression triggers.
 - At other times the block is doing nothing.
 - An object being assigned to must therefore remember the last value assigned (not continuously driven).
 - So, only “reg” type variables can be assigned within the “always” block.
 - Of course, any kind of variable may appear in the event expression (reg, wire, etc.).

Sequential Statements in Verilog

1. **begin**

sequential_statements

end

1. **if (expression)**

sequential_statement

[else

sequential_statement]

1. **case (expression)**

expr: sequential_statement

.....

default: sequential_statement

endcase

**begin...end
not required
if there
is only 1 stmt.**

1. forever

sequential_statement

1. repeat (expression)

sequential_statement

1. while (expression)

sequential_statement

1. for (expr1; expr2; expr3)

sequential_statement

1. # (time_value)

- Makes a block suspend for “time_value” time units.

2. @ (event_expression)

- Makes a block suspend until event_expression triggers.

// A combinational logic example

```
module mux21 (in1, in0, s, f);  
    input in1, in0, s;  
    output reg f;  
  
    always @ (*)  
        if (s)  
            f = in1;  
        else  
            f = in0;  
endmodule
```

// A sequential logic example

```
module dff_negedge (D, clock, Q, Qbar);  
    input  D, clock;  
    output reg Q, Qbar;  
  
    always @ (negedge clock)  
        begin  
            Q = D;  
            Qbar = ~D; // equiv. to Qbar = ~Q; in this example  
        end  
endmodule
```

// An incorrectly inferred sequential logic example

```
module incomp_state_spec (curr_state, flag);  
    input  [0:1] curr_state;  
    output reg [0:1] flag;  
  
    always @ (curr_state)  
        case (curr_state)  
            0, 1 : flag = 2;  
            3    : flag = 1;  
        endcase  
endmodule
```

The variable 'flag' is not assigned a value in all the branches of case.

➔ Latch is *inferred*

// A small change made

```
module incomp_state_spec (curr_state, flag);  
    input  [0:1] curr_state;  
    output [0:1] flag;  
    reg     [0:1] flag;  
  
    always @ (curr_state)  
        case (curr_state)  
            0, 1 : flag = 2;  
            3    : flag = 1;  
            default: flag = 0;  
        endcase  
endmodule
```

**'flag' defined for all
values of curr_state.
→ Latch is *avoided***

```

module ALU_4bit (f, a, b, op);

    input [1:0] op;
    input [3:0] a, b;
    output reg [7:0] f;

    parameter ADD=2'b00, SUB=2'b01,
              MUL=2'b10, DIV=2'b11;

    always @ (a or b or op)
        case (op)
            ADD : f = a + b;
            SUB : f = a - b;
            MUL : f = a * b;
            DIV  : f = a / b;
            default: f = 8'b0; // useful if any operand bit is x/z
        endcase
    endmodule

```

```
module priority_encoder (in, code);  
    input [0:3] in;  
    output reg [0:1] code;  
  
    always @ (in)  
        case (in)  
            in[0] : code = 2'b00;  
            in[1] : code = 2'b01;  
            in[2] : code = 2'd10;  
            in[3] : code = 2'b11;  
            default: code = 2'b0; // useful if any in[] bit is x/z  
        endcase  
    endmodule
```

Blocking & Non-blocking Assignments

- Sequential statements within procedural blocks (“always” and “initial”) can use two types of assignments:
 - Blocking assignment
 - Uses the ‘=’ operator
 - Non-blocking assignment
 - Uses the ‘<=’ operator

Blocking Assignment (using '=')

- Most commonly used type.
- The target of assignment gets updated before the next sequential statement in the procedural block is executed.
- A statement using blocking assignment blocks the execution of the statements following it, until it gets completed.
- Recommended style for modeling combinational logic.

Non-Blocking Assignment (using ' \leq ')

- The assignment to the target gets scheduled for the end of the simulation cycle.
 - Normally occurs at the end of the sequential block.
 - Statements subsequent to the instruction under consideration are not blocked by the assignment.
- Recommended style for modeling sequential logic.
 - Can be used to assign several 'reg' type variables synchronously, under the control of a common clock.

Some Rules to be Followed

- Verilog synthesizer ignores the delays specified in a procedural assignment statement.
 - May lead to functional mismatch between the design model and the synthesized netlist.
- A variable cannot appear as the target of *both* a blocking and a non-blocking assignment.
 - Following is not permissible:

```
value = value + 1;  
value <= init;
```

// Up-down counter (synchronous clear)

// with parallel load

```
module counter (mode, clr, ld, d_in, clk, count);  
    input mode, clr, ld, clk;  
    input [0:7] d_in;  
    output reg [0:7] count;  
  
    always @ (posedge clk)  
        if (ld)  
            count <= d_in;  
        else if (clr)  
            count <= 0;  
        else if (mode)  
            count <= count + 1;  
        else  
            count <= count - 1;  
endmodule
```

// Parameterized design:: an N-bit counter

module counter (clear, clock, count);

parameter N = 7;

input clear, clock;

output reg [0:N] count;

always @ (negedge clock)

if (clear)

count <= 0;

else

count <= count + 1;

endmodule

// Using more than one clocks in a module

```
module multiple_clk (clk1, clk2, a, b, c, f1, f2);  
    input  clk1, clk2, a, b, c;  
    output reg f1, f2;  
  
    always @ (posedge clk1)  
        f1 <= a & b;  
    always @ (negedge clk2)  
        f2 <= b ^ c;  
endmodule
```

// Using multiple edges of the same clock

module multi_phase_clk (a, b, f, clk);

input a, b, clk;

output reg f;

always @ (posedge clk)

f <= t & b;

always @ (negedge clk)

t <= a | b;

endmodule

A Ring Counter Example

```
module ring_counter (clk, init, count);  
    input  clk, init;  
    output reg [7:0] count;  
  
    always @ (posedge clk)  
    begin  
        if (init)  
            count <= 8'b10000000; // next: 00000001  
        else begin  
            count    <= count << 1;  
            count[0] <= count[7];  
        end  
    end  
  
end  
endmodule
```

A Ring Counter Example (Modified)

```
module ring_counter_modified (clk, init, count);  
    input  clk, init;  
    output reg [7:0] count;  
  
    always @ (posedge clk)  
    begin  
        if (init)  
            count <= 8'b10000000;  
        else  
            count <= {count[6:0], count[7]};  
    endmodule
```


About “Loop” Statements

- Verilog supports four types of loops:
 - ‘while’ loop
 - ‘for’ loop
 - ‘forever’ loop
 - ‘repeat’ loop
- Many Verilog synthesizers supports only ‘for’ loop for synthesis:
 - Loop bound must evaluate to a constant.
 - Implemented by unrolling the ‘for’ loop, and replicating the statements.

Modeling Memory

- Synthesis tools are usually not very efficient in synthesizing memory.
 - Best modeled as a component.
 - Instantiated in a design.
- Implementing memory as a two-dimensional register file is inefficient.

```
module memory_example (en, clk, adbus, dbus,  
                        rw);  
  
    parameter N = 16;  
    input  en, rw, clk;  
    input [N-1:0] adbus;  
    output [N-1:0] dbus;  
  
    .....  
    ROM Mem1 (clk, en, rw, adbus, dbus);  
  
    .....  
endmodule
```


Modeling Tri-state Gates

```
module bus_driver (in, out, enable);  
    input enable;          input [0:7] in;  
    output [0:7] out;      reg [0:7] out;  
  
    always @ (enable or in)  
        if (enable)  
            out = in;  
        else  
            out = 8'bz;  
endmodule;
```


Modeling Finite State Machines

- Two types of FSMs

- Moore Machine

 


- Mealy Machine

 

Moore Machine : Example 1

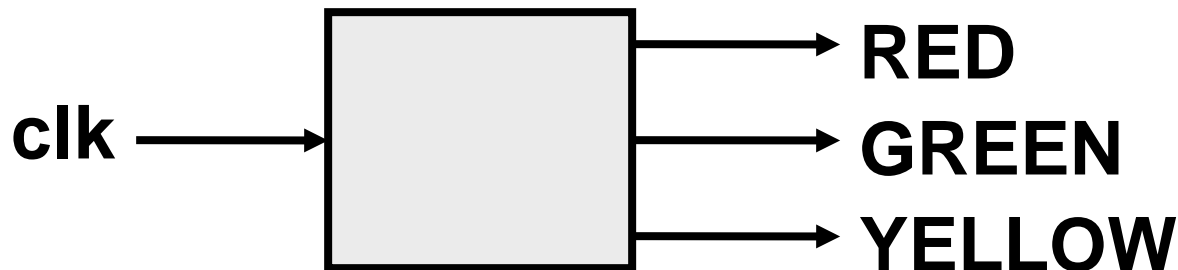- **Traffic Light Controller**
 - Simplifying assumptions made
 - Three lights only (RED, GREEN, YELLOW)
 - The lights glow cyclically at a fixed rate
 - Say, 10 seconds each
 - The circuit will be driven by a clock of appropriate frequency



```
module traffic_light (clk, light);  
    input clk;  
    output [0:2] light;    reg [0:2] light;  
    parameter S0=0, S1=1, S2=2;  
    parameter RED=3'b100, GREEN=3'b010,  
              YELLOW=3'b001;  
    reg [0:1] state;  
    always @ (posedge clk)  
        case (state)  
            S0: begin                                // S0 means RED  
                    light <= YELLOW;  
                    state <= S1;  
                end  
        end
```

```
S1: begin                                // S1 means YELLOW
    light <= GREEN;
    state <= S2;
end
S2: begin                                // S2 means GREEN
    light <= RED;
    state <= S0;
end
default: begin
    light <= RED;
    state <= S0;
end

endcase
endmodule
```

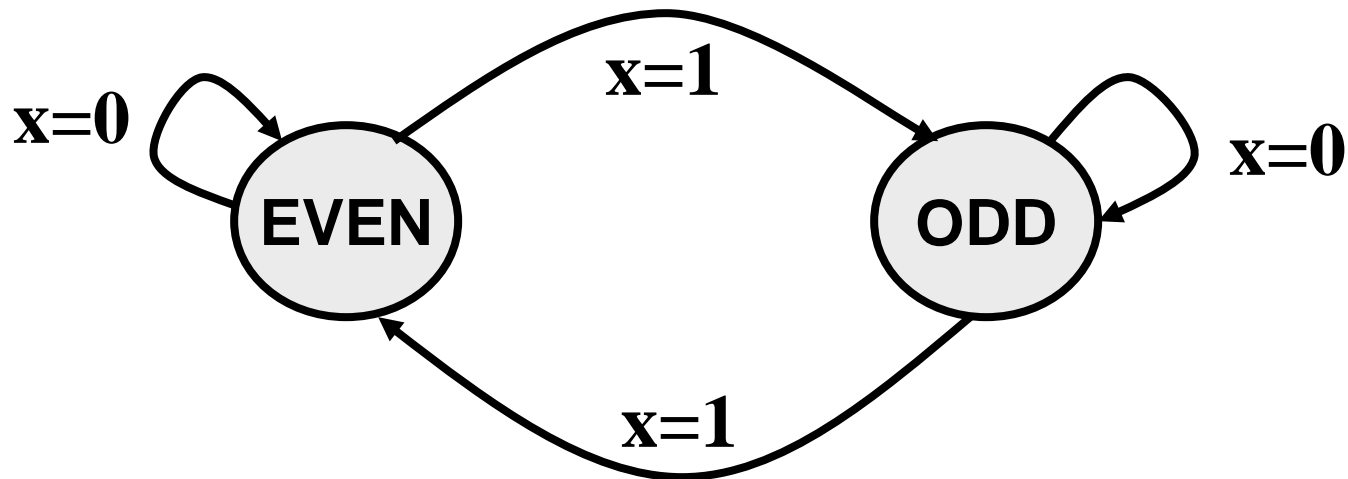
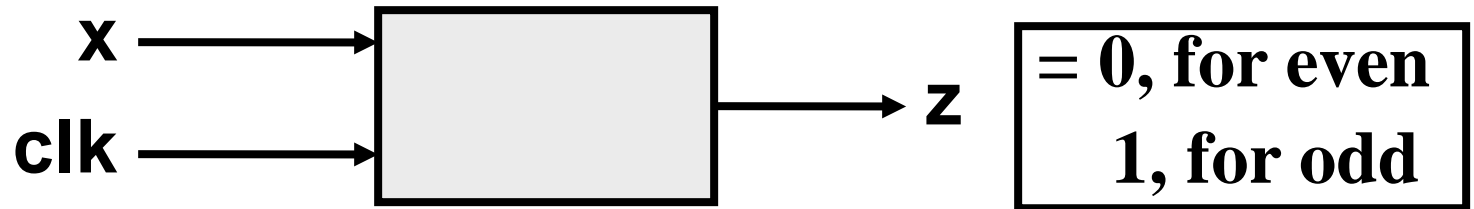

- **Comment on the solution**
 - **Five flip-flops are synthesized**
 - Two for 'state'
 - Three for 'light' (outputs are also latched into flip-flops)
 - **If we want non-latched outputs, we have to modify the Verilog code.**
 - Assignment to 'light' made in a separate 'always' block.
 - Use blocking assignment.

```
module traffic_light_nonlatched_op (clk, light);  
    input clk;  
    output [0:2] light;    reg [0:2] light;  
    parameter S0=0, S1=1, S2=2;  
    parameter RED=3'b100, GREEN=3'b010,  
              YELLOW=3'b001;  
    reg [0:1] state;  
    always @ (posedge clk)  
        case (state)  
            S0:    state <= S1;  
            S1:    state <= S2;  
            S2:    state <= S0;  
            default: state <= S0;  
        endcase
```

```
always @ (state)  
  case (state)  
    S0:      light = RED;  
    S1:      light = YELLOW;  
    S2:      light = GREEN;  
    default: light = RED;  
  endcase  
endmodule
```

Moore Machine: Example 2

- Serial parity detector




```
module parity_gen (x, clk, z);  
    input x, clk;  
    output z;    reg z;  
    reg even_odd; // The machine state  
    parameter EVEN=0, ODD=1;  
  
    always @ (posedge clk)  
        case (even_odd)  
            EVEN: begin  
                z <= x ? 1 : 0;  
                even_odd <= x ? ODD : EVEN;  
            end  
        end
```

```
    ODD: begin
        z <= x ? 0 : 1;
        even_odd <= x ? EVEN : ODD;
    end
endcase
endmodule
```

- If no output latches need to be synthesized, we can follow the principle shown in the last example.

Mealy Machine: Example

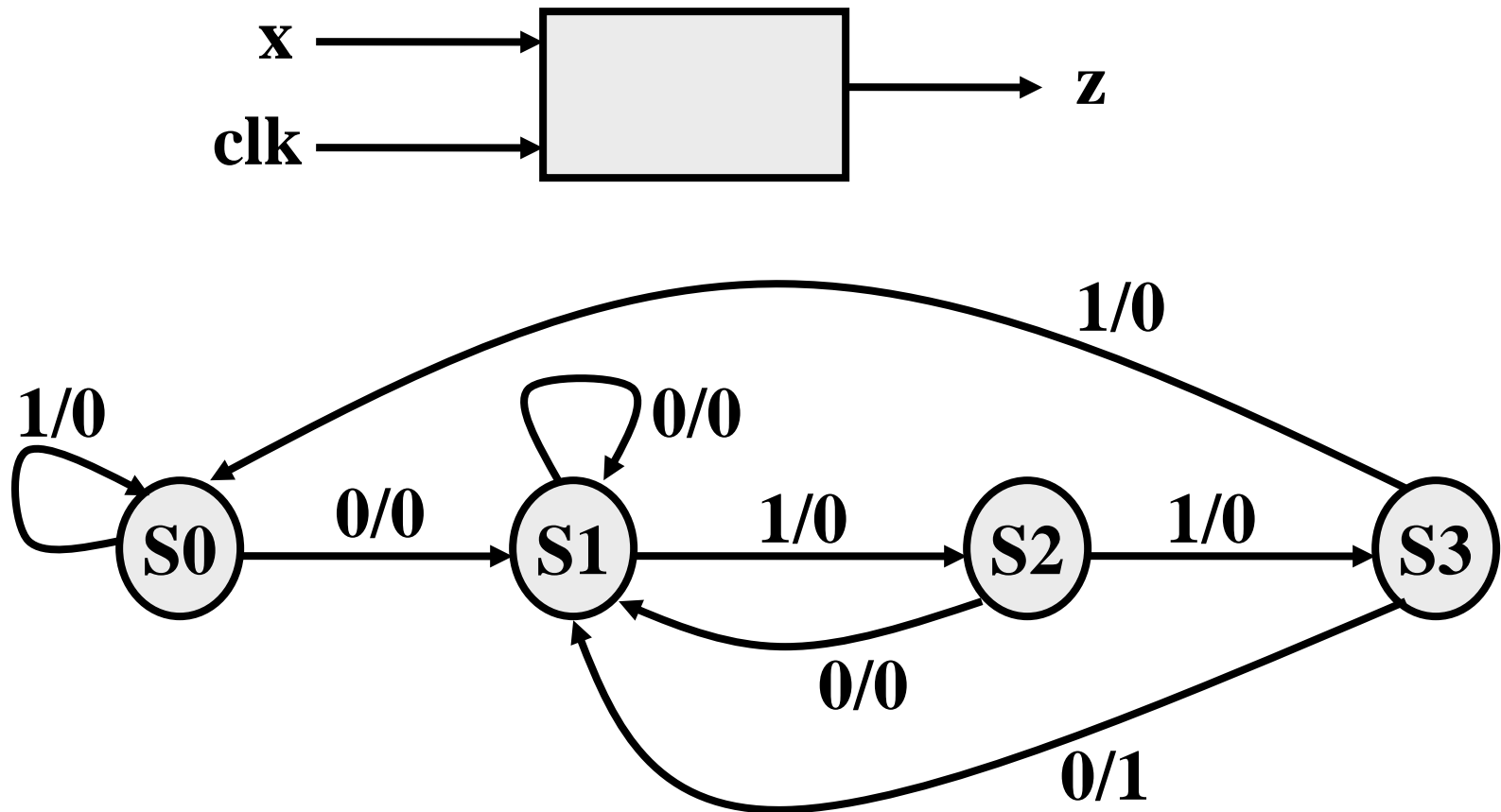- Sequence detector for the pattern '0110'.



S1 is the “accept state”, overlapped patterns allowed

0110110: 2 matches

01101111: 1 match

1111111: 0 match

// Sequence detector for the pattern '0110'

module seq_detector (x, clk, z)

input x, clk;

output reg z;

parameter S0=0, S1=1, S2=2, S3=3;

reg [0:1] PS, NS;

// sequential logic part

always @ (posedge clk)

PS <= NS;

// combinational logic part

always @ (*)

case (PS)

S0: begin

z = x ? 0 : 0;

NS = x ? S0 : S1;

end

S1: begin

z = x ? 0 : 0;

NS = x ? S2 : S1;

end

S2: begin

z = x ? 0 : 0;


NS = x ? S3 : S1;

end

```
S3: begin  
    z    = x ? 0 : 1;  
    NS = x ? S0 : S1;  
end  
endcase  
endmodule
```

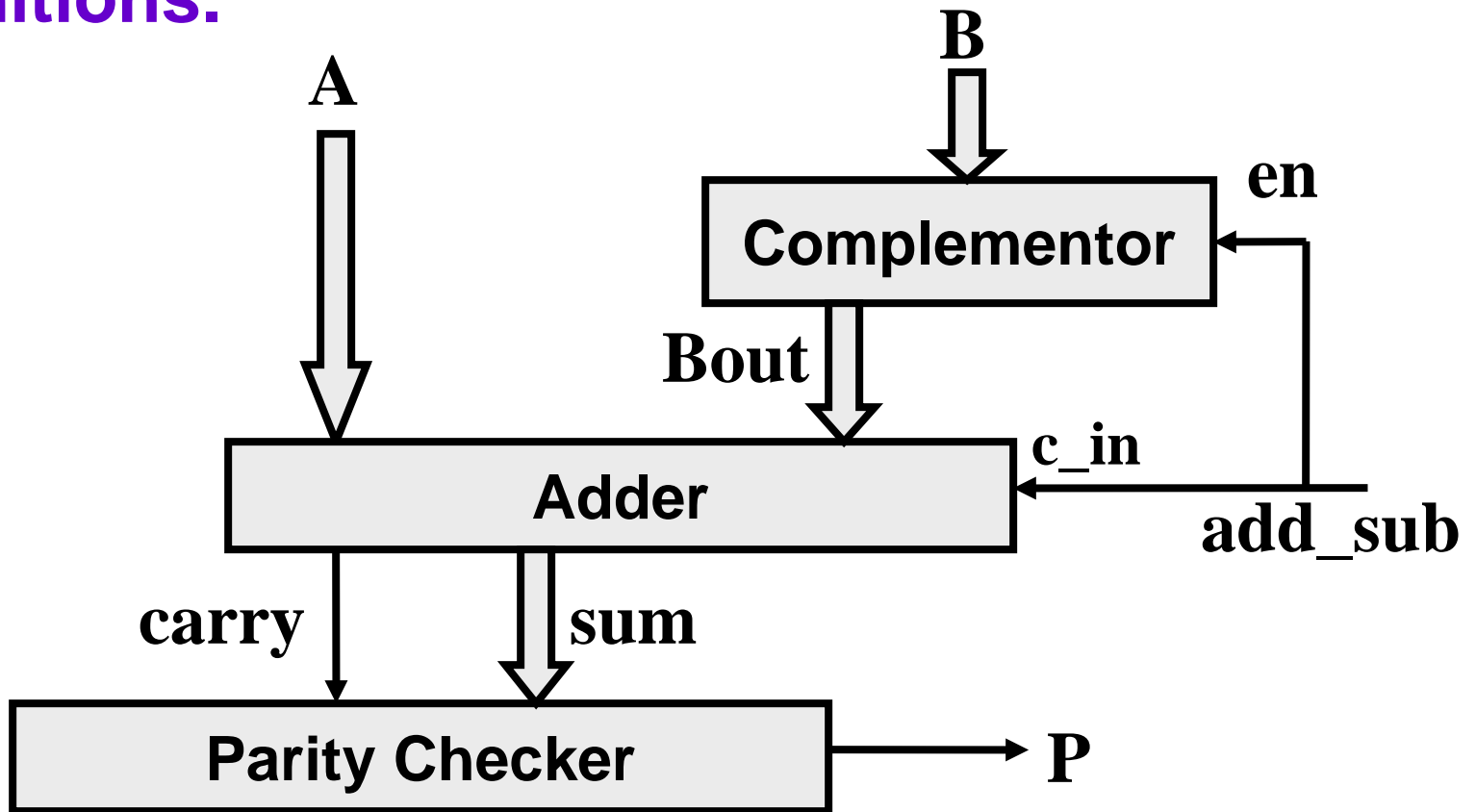Example with Multiple Modules

- A simple example showing multiple module definitions.



```
module complementor (Y, X, comp);  
    input [7:0] X;  
    input comp;  
    output [7:0] Y;    reg [7:0] Y;  
  
    always @ (X or comp)  
        if (comp)  
            Y = ~X;  
        else  
            Y = X;  
  
endmodule
```

```
module adder (sum, cy_out, in1, in2, cy_in);  
    input [7:0] in1, in2;  
    input cy_in;  
    output [7:0] sum;      reg [7:0] sum;  
    output cy_out;        reg cy_out;  
  
    always @ (in1 or in2 or cy_in)  
        {cy_out, sum} = in1 + in2 + cy_in;  
endmodule
```

```
module parity_checker (out_par, in_word);  
    input [8:0] in_word;  
    output out_par;  
  
    always @ (in_word)  
        out_par = ^ (in_word);  
endmodule
```

// Top level module

module add_sub_parity (p, a, b, add_sub);

input [7:0] a, b;

input add_sub; // 0 for add, 1 for subtract

output p; // parity of the result

wire [7:0] Bout, sum; wire carry;

complementor M1 (Bout, B, add_sub);

adder M2 (sum, carry, A, Bout, add_sub);

parity_checker M3 (p, {carry, sum});

endmodule

Memory Modeling Revisited

- Memory is typically included by instantiating a pre-designed module.
- Alternatively, we can model memories using two-dimensional arrays.
 - Array of register variables.
 - Behavioral model of memory.
 - Mostly used for simulation purposes.
 - For small memories, even for synthesis.

Typical Example

```
module memory_model ( ..... )
```

```
    reg [7:0]  mem [0:1023];
```

```
endmodule
```

How to Initialize memory

- By reading memory data patterns from a specified disk file.
 - Used for simulation.
 - Used in test benches.
- Two Verilog functions are available:
 1. \$readmemb (filename, memname, startaddr, stopaddr)
Data read in binary format.
 2. \$readmemh (filename, memname, startaddr, stopaddr)
Data read in hexadecimal format.

An Example

```
module memory_model ( ..... )  
    reg [7:0]  mem [0:1023];  
    initial  
        begin  
            $readmemh ("mem.dat", mem);  
        end  
endmodule
```

A Specific Example :: Single Port RAM with Synchronous Read-Write

```
module ram_1 (addr, data, clk, rd, wr, cs)
    input [9:0] addr;  input  clk, rd, wr, cs;
    inout [7:0] data;
    reg [7:0] mem [1023:0];  reg [7:0] d_out;

    assign data = (cs && rd) ? d_out ; 8'bz;
    always @ (posedge clk)
        if (cs && wr && !rd) mem [addr] = data;
    always @ (posedge clk)
        if (cs && rd && !wr) d_out = mem [addr];
endmodule
```

A Specific Example :: Single Port RAM with Asynchronous Read-Write

```
module ram_2 (addr, data, rd, wr, cs)
    input [9:0] addr;    input rd, wr, cs;
    inout [7:0] data;
    reg [7:0] mem [1023..0];    reg [7:0] d_out;


    assign data = (cs && rd) ? d_out ; 8'bz;
    always @ (addr or data or rd or wr or cs)
        if (cs && wr && !rd) mem [addr] = data;
    always @ (addr or rd or wr or cs)
        if (cs && rd && !wr) d_out = mem [addr];
endmodule
```

A Specific Example :: ROM/EPROM

```
module rom (addr, data, rd_en, cs)
    input [2:0] addr;  input rd_en, cs;
    output [7:0] data;
    reg [7:0] data;
    always @ (addr or rd_en or cs)
        case (addr)
            0:  22;
            1:  45;
            .....
            7:  12;
        endcase
endmodule
```

Verilog Test Bench

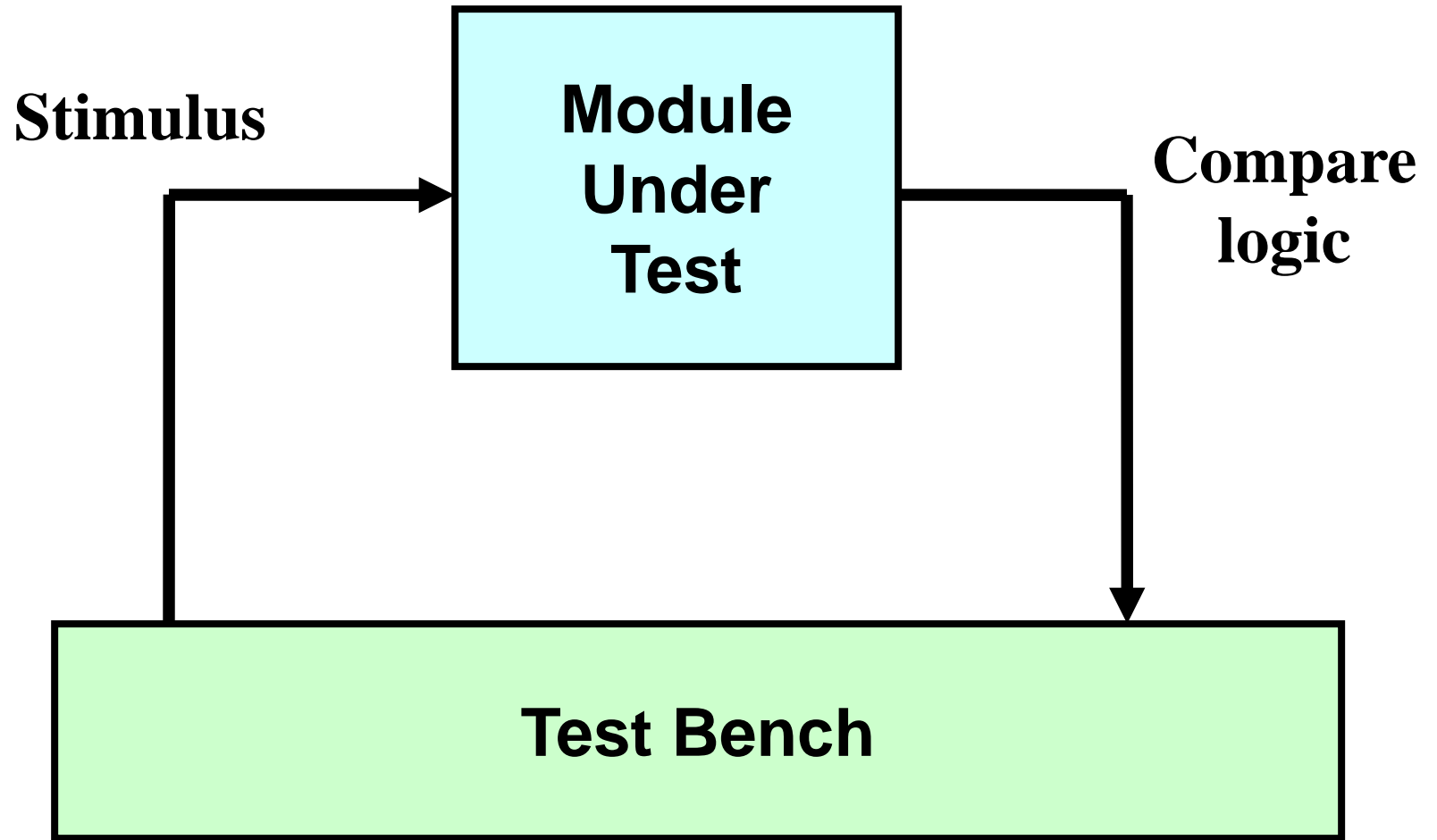- **What is test bench?**
 - A Verilog procedural block which executes only once.
 - Used for simulation.
 - Testbench generates clock, reset, and the required test vectors.



How to Write Testbench?

- **Create a dummy template**
 - Declare inputs to the module-under-test (MUT) as “reg”, and the outputs as “wire”
 - Instantiate the MUT.
- **Initialization**
 - Assign some known values to the MUT inputs.
- **Clock generation logic**
 - Various ways to do so.
- **May include several simulator directives**
 - Like \$display, \$monitor, \$dumpfile, \$dumpvars, \$finish.

- **\$display**
 - Prints text or variables to stdout.
 - Syntax same as “printf”.
- **\$monitor**
 - Similar to \$display, but prints the value whenever the value of some variable in the given list changes.
- **\$finish**
 - Terminates the simulation process.
- **\$dumpfile**
 - Specify the file that will be used for storing the waveform.
- **\$dumpvars**
 - Starts dumping all the signals to the specified file.

Example Testbench

```
module shifter_toplevel;  
    reg clk, clear, shift;  
    wire [7:0] data;  
  
    shift_register S1 (clk, clear, shift, data);  
    initial  
        begin  
            clk = 0;  clear = 0;  shift = 0;  
        end  
    always  
        #10 clk = !clk;  
endmodule
```

Testbench: More Complete Version

```
module shifter_toplevel;  
    reg clk, clear, shift;  
    wire [7:0] data;  
  
    shift_register S1 (clk, clear, shift, data);  
    initial  
        begin  
            clk = 0;  clear = 0;  shift = 0;  
        end  
    always  
        #10 clk = !clk;
```

contd..

```
initial
begin
    $dumpfile ("shifter.vcd");
    $dumpvars;
end
initial
begin
    $display ("\ttime, \tclk, \tclr, \tsft, \tdata);
    $monitor ("%d, %d, %d, %d, %d", $time,
        clk, reset, clear, shift, data);
end
initial
    #400 $finish;
***** REMAINING CODE HERE *****
endmodule
```

A Complete Example

```
module testbench;  
    wire w1, w2, w3;  
    xyz m1 (w1, w2, w3);  
    test_xyz m2 (w1, w2, w3);  
endmodule
```

```
module xyz (f, A, B);  
    input A, B;    output f;  
    nor #1 (f, A, B);  
ndmodule
```

contd..

```
module test_xyz (f, A, B);  
    input f;  
    output A, B;  
    reg A, B;  
    initial  
        begin  
            $monitor ($time, "A=%b", "B=%b", f=%b",  
                    A, B, f);  
  
            #10 A = 0; B = 0;  
            #10 A = 1; B = 0;  
            #10 A = 1; B = 1;  
            #10 $finish;  
        end  
    endmodule
```